

<i>Application Note</i>	<i>THAN0064_Rev1.40_E</i>
-------------------------	---------------------------


**THC63LVD103(D)/THC63LVD105/THC63LVD104S(C)**  
**ApplicationNote**  
System Diagram and PCB Design Guide Line

## Contents

1.TTL Data Timing Diagram .....	P3
2.LVDS DATA Timing Diagram .....	P4
3.Example of System Diagram	
1)10 bit TTL/CMOS Level Input .....	P5
2)10 bit Small Swing Level Input .....	P6
3)8 bit TTL/CMOS Level Input .....	P7
4.NOTE .....	P8,9
5. PCB Design Guide Line for LVDS .....	P10
 
## 1. TTL DATA Timing Diagram


Following are THC63LVD103(D)/THC63LVD105 TTL data input timing example for SXGA+(1400 x 1050).



Note:

	Red	Green	Blue
MSB	R9	G9	B9
	R8	G8	B8
	R7	G7	B7
	R6	G6	B6
	R5	G5	B5
6bit LSB	R4	G4	B4
	R3	G3	B3
8bit LSB	R2	G2	B2
	R1	G1	B1
10bit LSB	R0	G0	B0

## 2.LVDS DATA Timing Diagram

 

THC63LVD103(D)/THC63LVD105/THC63LVD104S(C) Pixel Data Assign (6bit,8bit,10bit Application)

	6bit	8bit	10bit
TA0	R4	R4	R4
TA1	R5	R5	R5
TA2	R6	R6	R6
TA3	R7	R7	R7
TA4	R8	R8	R8
TA5	R9	R9	R9
TA6	G4	G4	G4
TB0	G5	G5	G5
TB1	G6	G6	G6
TB2	G7	G7	G7
TB3	G8	G8	G8
TB4	G9	G9	G9
TB5	B4	B4	B4
TB6	B5	B5	B5
TC0	B6	B6	B6
TC1	B7	B7	B7
TC2	B8	B8	B8
TC3	B9	B9	B9
TC4	Hsync	Hsync	Hsync
TC5	Vsync	Vsync	Vsync
TC6	DE	DE	DE
TD0	-	R2	R2
TD1	-	R3	R3
TD2	-	G2	G2
TD3	-	G3	G3
TD4	-	B2	B2
TD5	-	B3	B3
TD6	-	N/A	N/A
TE0	-	-	R0
TE1	-	-	R1
TE2	-	-	G0
TE3	-	-	G1
TE4	-	-	B0
TE5	-	-	B1
TE6	-	-	N/A

Note:For 6bit application,use A~C channel and open TD+/-,TE+/- pin.  
For 8bit application,use A~D channel and open TE+/- pin.


### 3. Example of System Diagram

#### 1) 10 bit TTL/CMOS Input

Example:

THC63LVD103(D)/THC63LVD105 :Falling edge/Normal swing

THC63LVD104S(C) :Falling edge

 

\*1: If RS pin is tied to VCCTX, LVDS swing is 350mV.

If RS pin is tied to GND, LVDS swing is 200mV.

\*2: Connect each PCB GND


\*3: THC63LVD104S = 2.5V  
THC63LVD104C = 3.3V

## 2)10 bit Small Swing Level Input


Example:

THC63LVD103(D)/THC63LVD105 :Falling edge/Normal swing

THC63LVD104S(C) :Falling edge

 

 \*1:RS pin acts as VREF input pin when input voltage is set to half of high level signal input.



Example for Small Swing input (R1,R2)=(3.3kohm,1kohm~2.2kohm)


\*2:Connect each PCB GND

\*3: THC63LVD104S = 2.5V  
THC63LVD104C = 3.3V

### 3) 8 bit TTL/CMOS Level Input

 Example:

THC63LVD103(D)/THC63LVD105 :Small Swing input/Falling edge/Small swing  
THC63LVD104S(C) :Falling edge



\*1: If RS pin is tied to VCCTX, LVDS swing is 350mV.  
If RS pin is tied to GND, LVDS swing is 200mV.

\*2: Connect each PCB GND

\*3: THC63LVD104S = 2.5V  
THC63LVD104C = 3.3V

\*4

THC63LVD104S	THC63LVD104C
VCCRX (2.5V) 820ohm — RE- 100ohm — RE+ 470ohm — GND	OPEN — RE- OPEN — RE+

## 4. Note

### 1) Output Control

THC63LVD103(D)/THC63LVD105

/PDWN	Input(TTL)	Output(LVDS)
L	Open or Hi-z	Hi-z
L	Input CLK	Hi-z
H	Open or Hi-z	Hi-z
H	Input CLK *1	Data, CLK Out

THC63LVD104S(C)

PD	OE	Input(LVDS)	Output(TTL)
L	L	Open or Hi-z	Hi-z
L	L	Input CLK	Hi-z
L	H	Open or Hi-z	All Low
L	H	Input CLK	All Low
H	L	Open or Hi-z	Hi-z
H	L	Input CLK	Hi-z
H	H	Open or Hi-z	All Low
H	H	Input CLK *1	Data, CLK Out

\*1 Within the range of Recommended Operating Conditions. Refer to Recommended Operating Conditions on data sheet. Without the range, each Output(TTL) signal is unfixed Data, CLK Out.

### 2) Power On Sequence

Power on THC63LVD103(D)/THC63LVD105 after THC63LVD104S(C). If it is not avoidable, please contact to

mspsupport@thine.co.jp (for FAE mailing list)

### 3) Cable Connection and Disconnection


Don't connect and disconnect the LVDS cable, when the power is supplied to the system.

### 4) GND Connection

Connect the each GND of the PCB which THC63LVD103(D)/THC63LVD105 and THC63LVD104S(C) on it. It is better for EMI reduction to place GND cable as close to LVDS cable as possible.
 
## 5) Multi Drop Connection





Multi drop connection is not recommended.


    
## 6) Asynchronous use

Asynchronous use such as following systems are not recommended. If it is not avoidable, please contact to

[mspsupport@thine.co.jp](mailto:mspsupport@thine.co.jp) (for FAE mailing list)




## 5. PCB Design Guide Line

### General Guideline

- Use 4 layer PCB (minimum).
- Locate by-pass capacitors adjacent to the device pins as close as possible.
- Make the loop minimum which is consist of Power line and Gnd line.
 
### LVDS Traces

- Interconnecting media between Transmitter and Receiver (i.e. PCB trace, connector, and cable) should be well balanced.(Keep all these differential impedance and the length of media as same as possible.).
- Minimize the distance between traces of a pair ( $S_1$ ) to maximize common mode rejection. See following figure.
- Place adjacent LVDS trace pair at least twice ( $>2 \times S_1$ ) as far away as much as possible.
- Avoid 90 degree bends.
- Minimize the number of VIA on LVDS traces.
- Match impedance of PCB trace, connector, media (cable) and termination to minimize reflections (emissions) for cabled applications (typically 100ohm differential mode characteristic impedance).
- Place Terminal Resister adjacent to the Receiver.



## Attentions and Requests

1. The product specifications described in this material are subject to change without prior notice.
2. The circuit diagrams described in this material are examples of the application which may not always apply to the customer's design. We are not responsible for possible errors and omissions in this material. Please note if errors or omissions should be found in this material, we may not be able to correct them immediately.
3. This material contains our copy right, know-how or other proprietary. Copying or disclosing to third parties the contents of this material without our prior permission is prohibited.
4. Note that if infringement of any third party's industrial ownership should occur by using this product, we will be exempted from the responsibility unless it directly relates to the production process or functions of the product.
5. This product is presumed to be used for general electric equipment, not for the applications which require very high reliability (including medical equipment directly concerning people's life, aerospace equipment, or nuclear control equipment). Also, when using this product for the equipment concerned with the control and safety of the transportation means, the traffic signal equipment, or various Types of safety equipment, please do it after applying appropriate measures to the product.
6. Despite our utmost efforts to improve the quality and reliability of the product, faults will occur with a certain small probability, which is inevitable to a semi-conductor product. Therefore, you are encouraged to have sufficiently redundant or error preventive design applied to the use of the product so as not to have our product cause any social or public damage.
7. Please note that this product is not designed to be radiation-proof.
8. Customers are asked, if required, to judge by themselves if this product falls under the category of strategic goods under the Foreign Exchange and Foreign Trade Control Law.

**THine Electronics, Inc.**  
E-mail: sales@thine.co.jp